
Discussion 7: Handshake Synchronizer and SHA-256

ECE 111: Advanced Digital Design Project
Fall 2024


(Courtesy: Vishal Karna)

Announcements

- Final Project Part1 released. It includes:
 - Part-1 : Develop Handshake Synchronizer RTL model
 - Part-2 : Develop SHA256 RTL model
- Due Date: 27 Nov, 2024 (Max 2 late days allowed; 20% grade reduction per late day).
- HW6 due today (13 Nov, 2024). Late due date 15 Nov, 2024.

Handshake Synchronizer


Clock Domain Crossing (CDC)

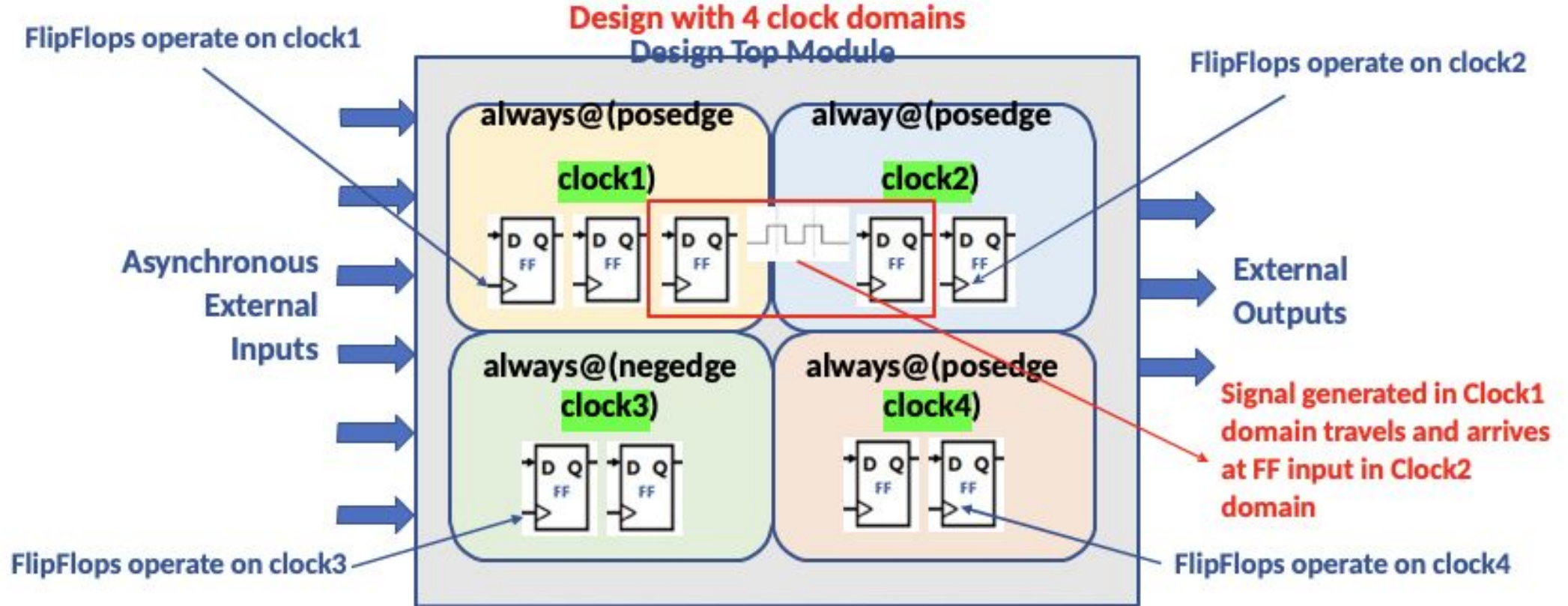

❑ What is Clock Domain Crossing (CDC) ?

- Signal travels from one clock domain to another clock domain
- CDC takes place anytime the inputs to a given flipflop were set based upon some other clock
- In example above signal generated from FF operating on clock1 travels and arrives at the flipflop inputs which is operating on clock2 → **Signal crossed clock domains**

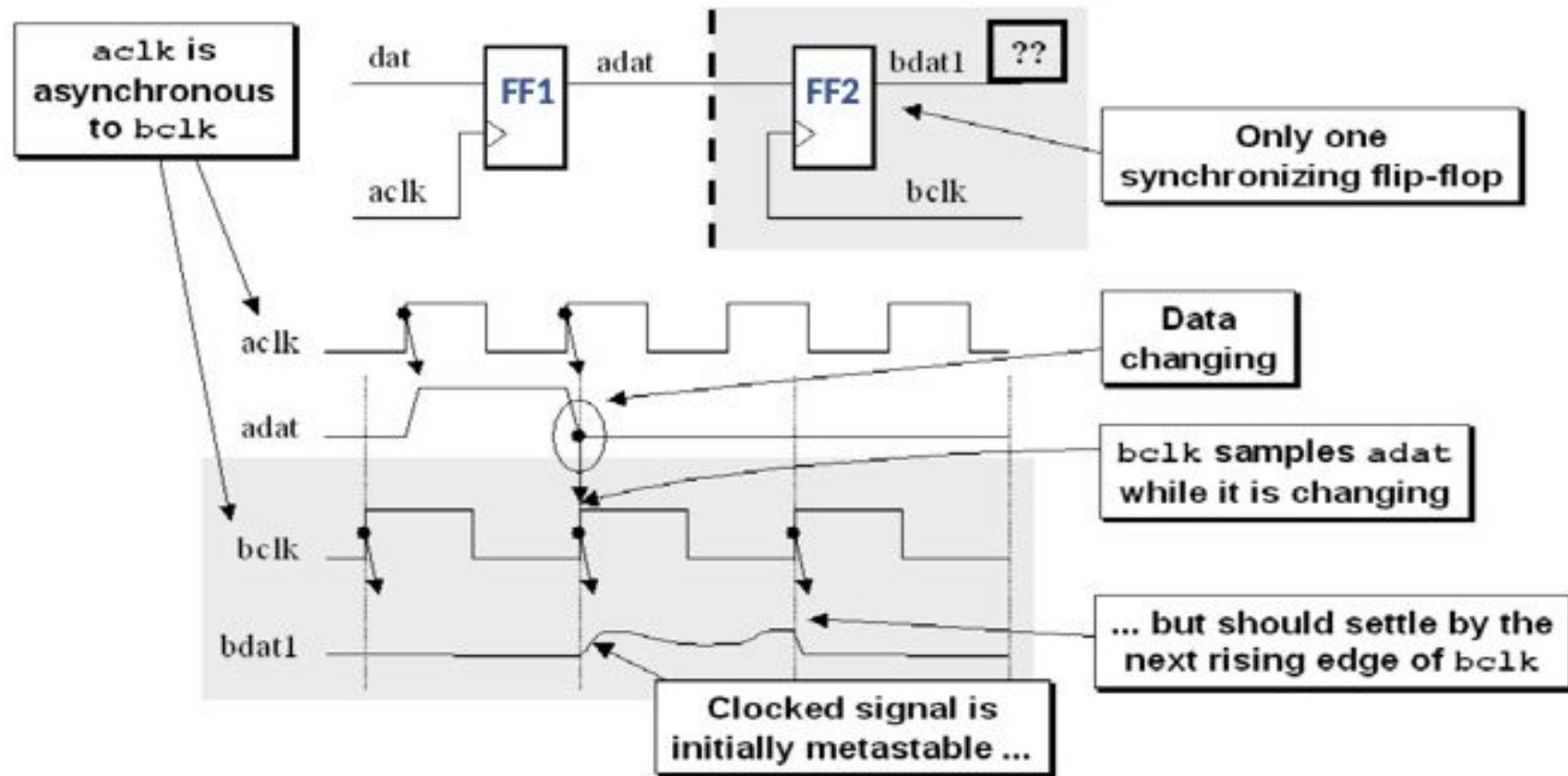What is the issue when signal crosses clock domains ?



- ❑ Synchronization failure that occurs when a signal (**adat**) generated in one clock domain (**aclk**) is sampled too close to the rising edge of a clock signal (**bclk**) from a second clock domain.
- ❑ **adat does not meet setup time requirement for FF2 hence output of FF2 (**bdat1**) goes metastable**
 - output (**bdat1**) going metastable and not converging to a legal stable state by the time the output must be sampled again.

Synchronization Techniques



- ❑ **Open-loop and Close-loop Synchronization**

- ❑ **For Single-bit control signal synchronization :**
 - 2-FF or 3-FF Synchronizer (open-loop)

- ❑ **For Multi-bit data bus synchronization :**
 - Handshake Mechanism (closed loop)
 - Asynchronous FIFO (open loop)



Signal Crossing Slow Clock Domain to Fast Clock Domain

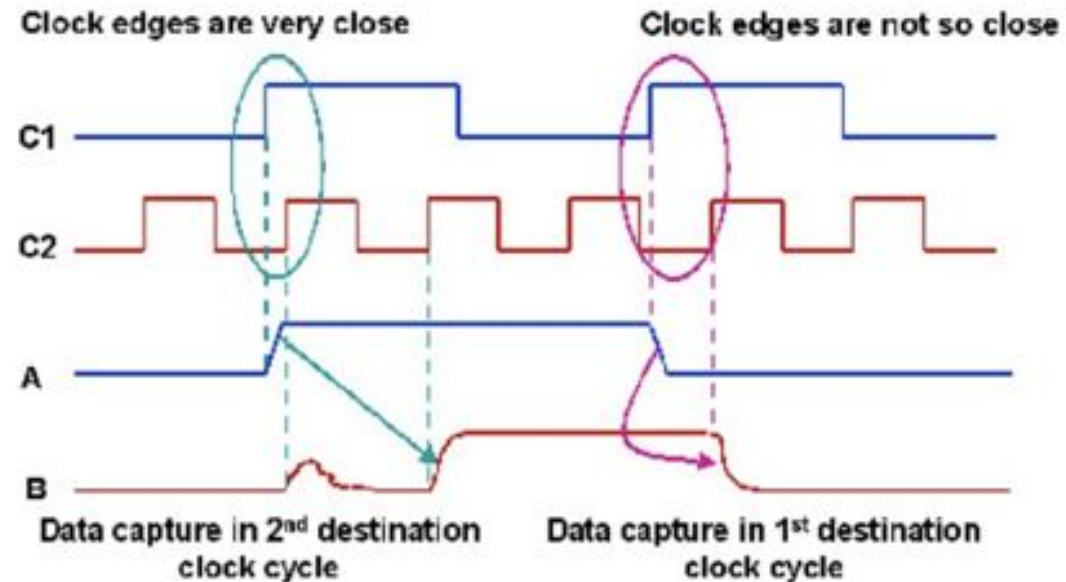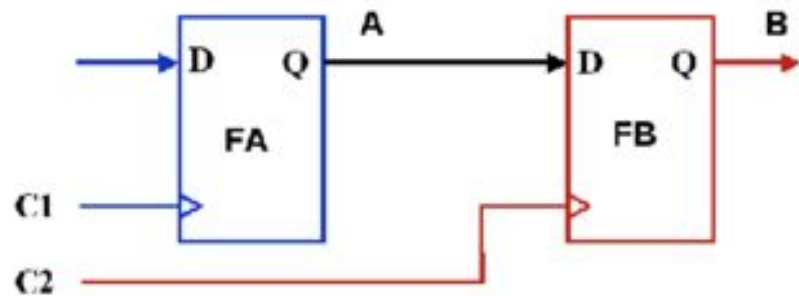❑ Scenario -1 : Flipflop-A clock frequency < Flipflop-B clock frequency



- ❑ If the transition on signal A happens very close to the active edge of clock C2, it could lead to setup or hold violation at the destination flop "FB" and "FB" will enter metastable state.
- ❑ Output signal B from FA will be unstable and may or may not settle down to some stable value before the next clock edge of C2 arrives
- ❑ Unstable signal B fanout cones may read different values, and may cause the design to enter into an unknown functional state, leading to functional issues in the design
- ❑ **To address such slow to fast clock domain crossing scenario, two or three flipflop synchronizer can be used !**

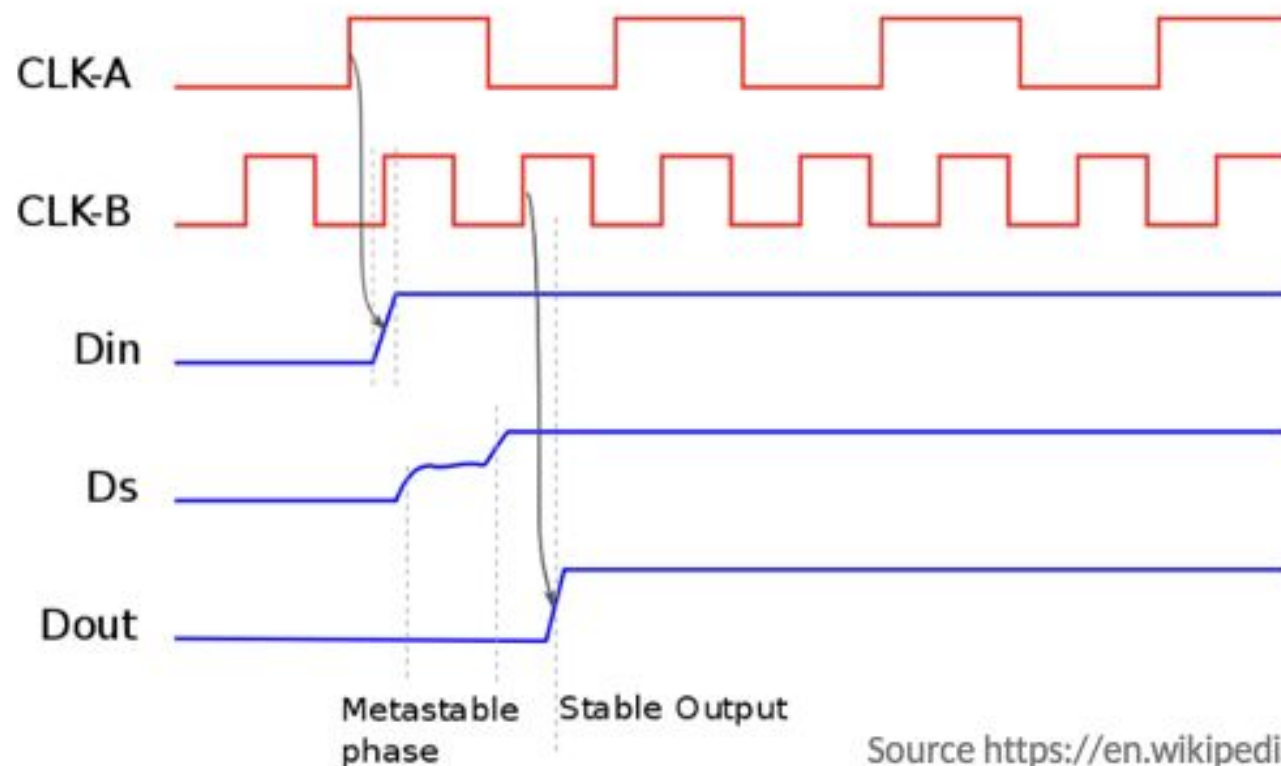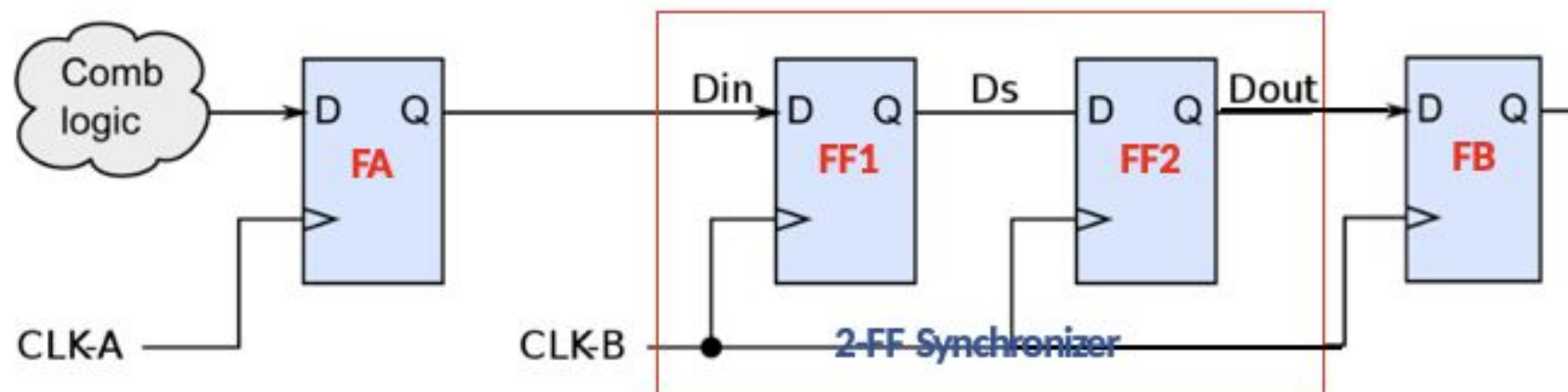
2-FlipFlop Synchronizer For Slow to Fast Clock Domain



- ❑ CLK-A frequency is slower than CLK-B
- ❑ Din entering into CLK-B domain goes through 2-FF synchronizer stage (FF1, FF2)
- ❑ 2-FF synchronizer will operate on receiving clock which is CLK-B
- ❑ Even if Din changes close to CLK-B clock edge violating setup violation of FF1, causing metastable output Ds, output of second stage of synchronizer (FF2) will be stable.
- ❑ If Din changes fast and frequently, sometimes 2-FF synchronizer is not enough for metastable output to settle. In such cases 3rd FF can be added (i.e. 3-FF synchronizer)

Signal Crossing Fast Clock Domain to Slow Clock Domain

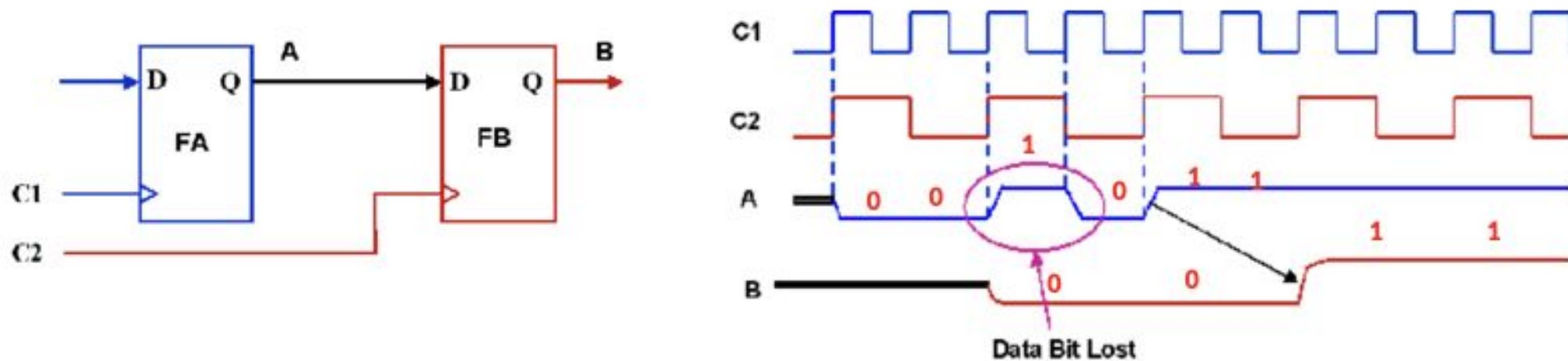
❑ **Scenario-2 : Flipflop-A clock frequency > Flipflop-B clock frequency**



- ❑ C1 is two times faster than C2 and there is no phase difference between C1 and C2
- ❑ If signal A is changing rapidly, say for example signal A sequence is "001011", output from FB in C2 clock domain will be "0011".
 - Here the third data value in the input sequence which is "1" is lost → data loss
 - For some circuits data loss is not acceptable
- ❑ **Two or three Flipflop synchronizer technique will avoid data loss, instead either of the techniques can be used to avoid data loss when data is sent from fast to slow clock domain :**
 - Storage between FA and FB (Asynchronous FIFO)
 - Handshake Synchronization technique between FA and FB


2-FF Synchronizer for Signal crossing Fast Clock to Slow Clock Domain

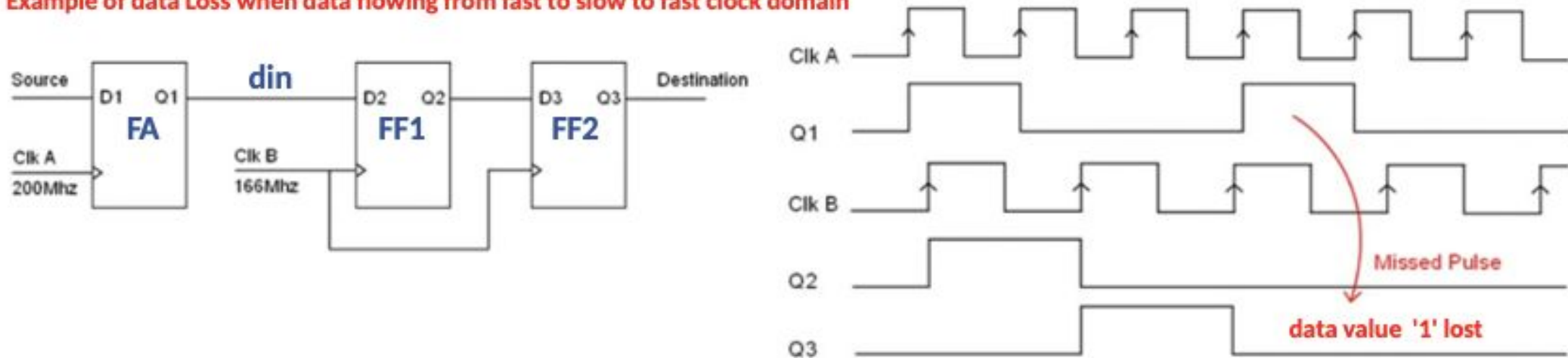Example of data Loss when data flowing from fast to slow to fast clock domain




- ❑ Consider, signal crossing from source clock domain ClkA to Destination ClkB domain where ClkA is faster than ClkB
- ❑ ClkA is 200 Mhz and Clk B is 166 MHz
- ❑ Signal is Crossing Fast to Slow clock domain through 2-FF synchronizers (FF1 and FF2)
- ❑ Adding 2-FF or 3-FF synchronizer will still result in data loss when signal crossed fast to slow clock domain as seen in the waveform above
- ❑ If source signal “din” width entering FF1 can be guaranteed to be 1.5 times of receiving clock ClkB then 2-FF or 3-FF synchronizer still can be used for signals crossing fast to slow clock domain
- ❑ If source signal cannot be guaranteed to 1.5 times of receiving clock and if the data loss is not acceptable for subsequent circuit in destination clock domain **then 2-FF or 3-FF open ended synchronization technique should not be deployed !**

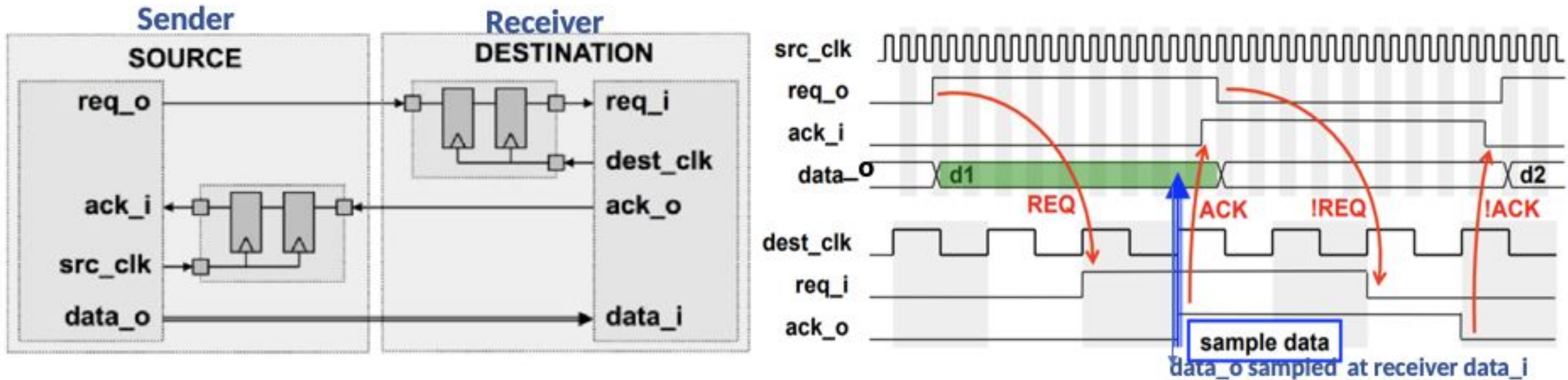Handshake Synchronizer For Multi-bit Signal Crossing Fast to Slow Clock Domain




- ❑ For many open-ended data-passing applications, a simple **req-ack** handshaking sequence is sufficient
- ❑ The sender places data onto a data bus (**data_o**) and then synchronizes a "**req_o**" signal (request) to the receiving clock domain.
- ❑ When the "**req_o**" signal is recognized in the destination clock domain, the receiver clocks the `data_o` into a register (the data should have been stable for at least two/three sampling clock edges in the destination clock domain)
- ❑ Receiver then passes an "**ack_o**" signal (acknowledgement) through a synchronizer to the sender.
- ❑ When the sender recognizes the synchronized "**ack_o**" signal, the sender can change the value being driven onto the data bus (**data_o**)

Homework : Handshake Synchronizer

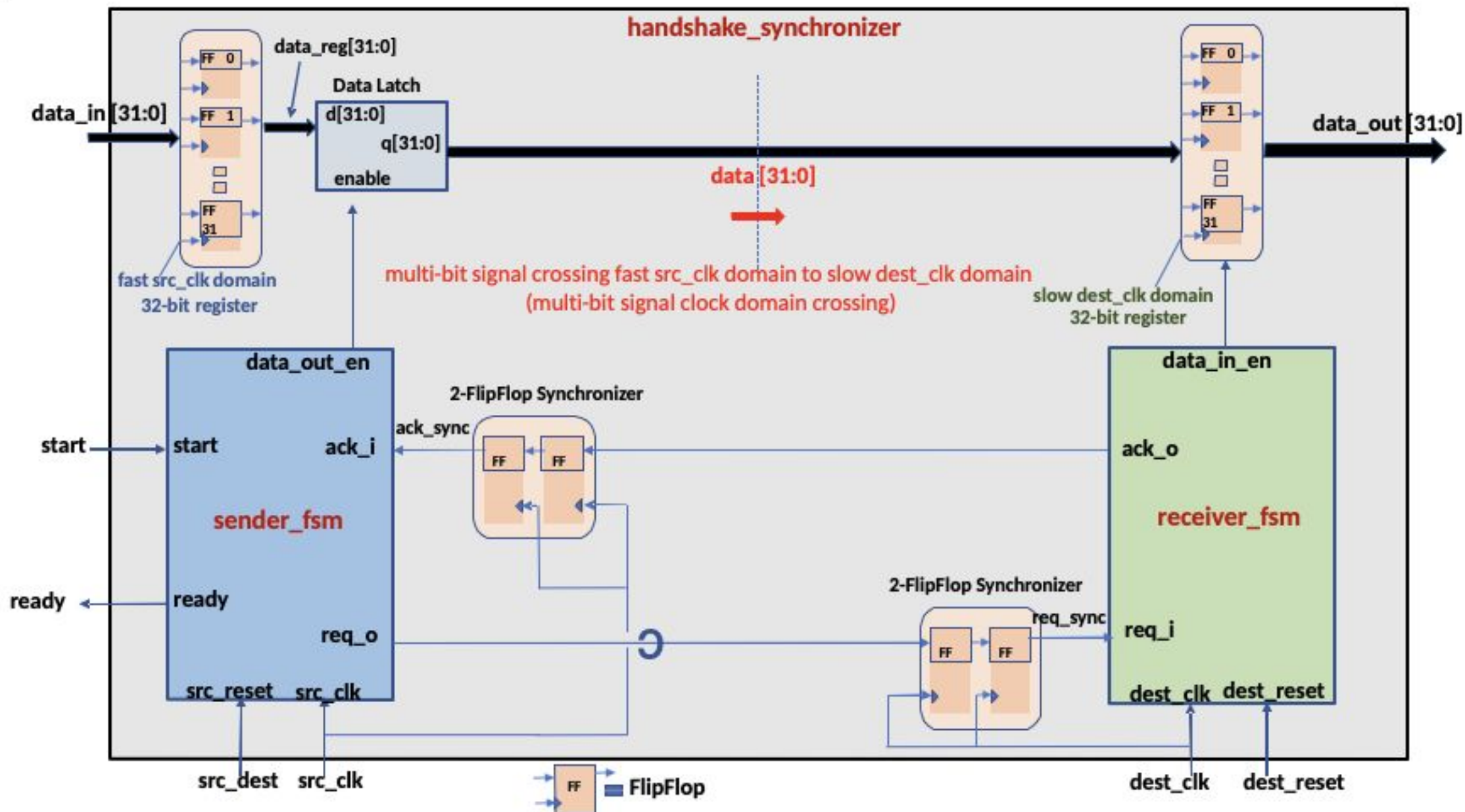

Homework : Handshake Sender FSM


Handshake Sender FSM

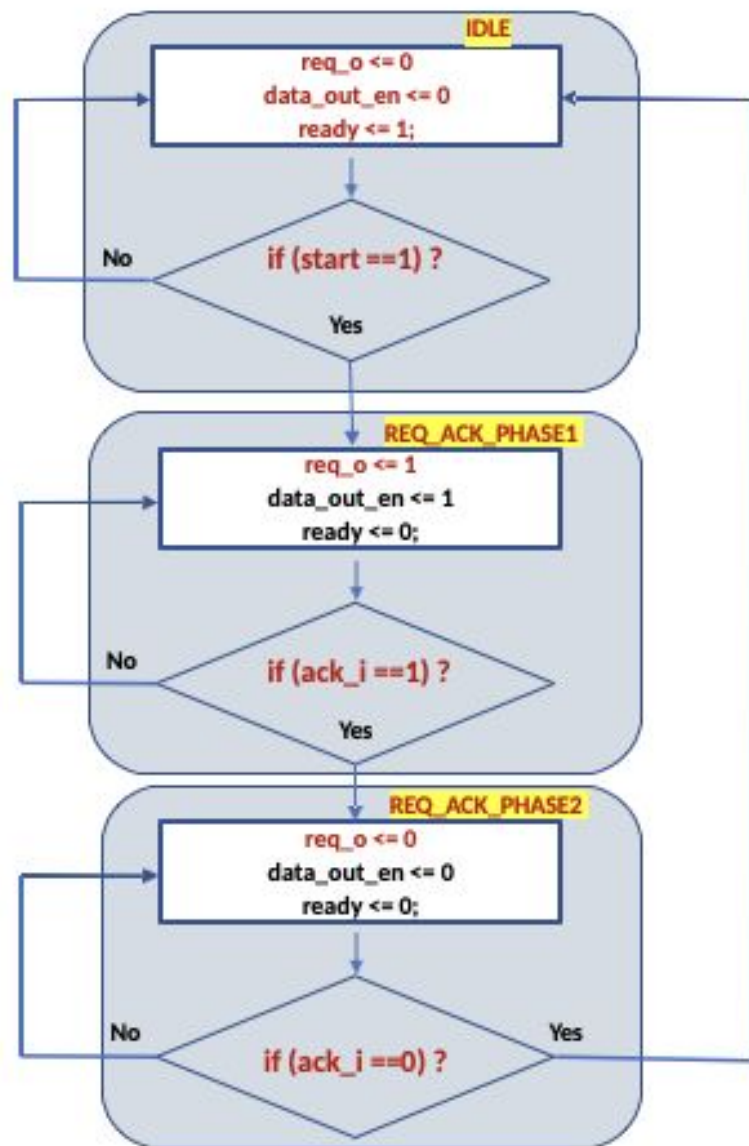

- **Purpose :** Sends data from faster `src_clk` domain to slower `dest_clk` domain using `req ack` handshake protocol. Holds data until `dest_clk` domain `receiver_fsm` has not acknowledged acceptance of data. Once data is accepted by `receiver_fsm`, then `sender_fsm` gets ready to send next data to `dest_clk` domain
- **IDLE State :**
 - Asserts `ready = 1` indicating testbench that handshake `sender_fsm` is ready to receive next 32-bit data
 - Waits for `start == 1` from testbench, which indicates next 32-bit data is available to be sent to `dest_clk` domain. And then move to REQ_ACK_PHASE1
- **REQ_ACK_PHASE1 :**
 - Asserts `req_o` and `data_out_en` to '1' which indicates request is available for `receiver_fsm` to accept
 - Then waits for `ack_i == 1` from `receiver_fsm` and then moves to REQ_ACK_PHASE2 once request acceptance has been acknowledged
- **REQ_ACK_PHASE2 :**
 - De-asserts `req_o` and `data_out_en` to '0' since `receiver_fsm` has captured 32-bit data
 - Then waits for `ack_i == 0` from `receiver_fsm` which is indication that `receiver_fsm` is now ready to receive next 32 bit data from `src_clk` domain and then moves to IDLE state

Homework : Handshake Receiver FSM


Handshake Receiver FSM

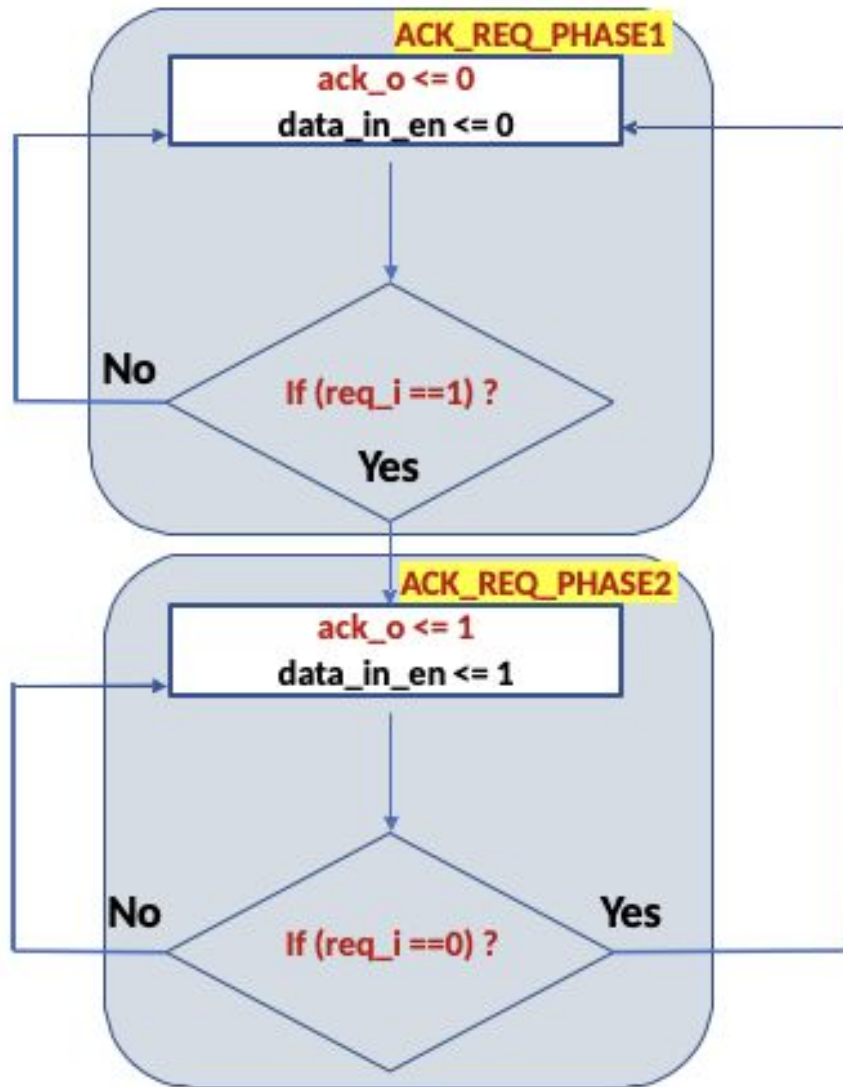

- **Purpose :** Receive data from fast `src_clk` domain and capture it in slow `dest_clk` domain register (flipflop) using req ack handshake protocol. Provides acknowledgement to `receiver_fsm` once data is captured in the destination register (flipflop)
- **ACK_REQ_PHASE1 :**
 - De-asserts `ack_o` and `data_in_en` to '0' and then waits for `req_i == 1`
 - This indicates to `sender_fsm` that it is ready to receive next 32 bit data and then moves to ACK_REQ_PHASE2
- **ACK_REQ_PHASE2 :**
 - Asserts `ack_o` and `data_in_en` to '1' which indicates 32-bit data from `src_clk` domain `sender_fsm` has been captured in `dest_clk` domain
 - Then waits for `req_i == 0` from handshake `sender_fsm` and then moves to REQ_ACK_PHASE1 to complete acknowledgement handshake protocol

Homework: Handshake Synchronizer

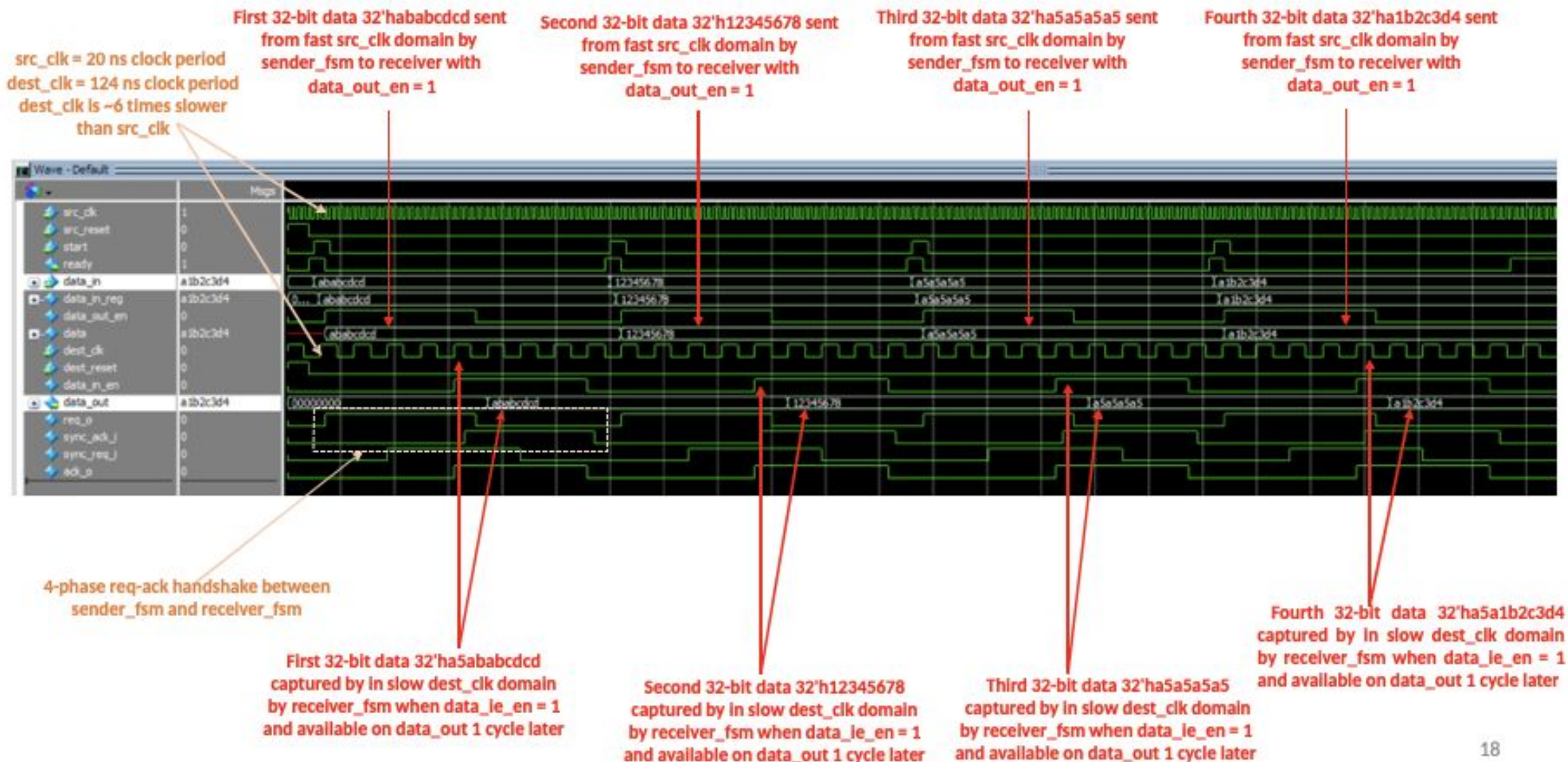
Reference simulation waveform for handshake_synchronizer module



SHA-256

Cryptographic hashing functions

 - Cryptographic hashing functions are functions or algorithms to convert input data of arbitrary size, called message, into a fixed-size output, called hash value or message digest




- Secure cryptographic hash functions have the following properties:
 - Compression
 - Avalanche Effect
 - Determinism
 - Pre-Image Resistant (One Way Function)
 - Collision Resistance
 - Efficient (Quick Computation)

Secure Hash Algorithm (SHA)

- SHA is family of cryptographic hash functions designed by the United States National Security Agency (NSA) and published by the United States National Institute of Standards and Technology (NIST)
- There are multiple SHA Algorithms:
 - SHA-1 : Input message up to 2^{64} bits produces 160-bit output hash value (a.k.a message digest)
 - SHA-2 : Input message up to 2^{64} bits produces 256-bit output hash value
 - consists of six hash functions with digests with 224, 256, 384 or 512 bits: SHA-224, SHA-256, SHA-384, SHA-512, SHA-512/224, SHA-512/256.
 - SHA-3 : Input message of up to 2^{128} bits produces 512-bit output hash value
- SHA-256 General Assumptions:
 - Input message must be $\leq 2^{64}$ bits
 - Message is processed in 512-bit blocks sequentially
 - Message digest (output hash value) is 256 bits

SHA-256 Algorithm

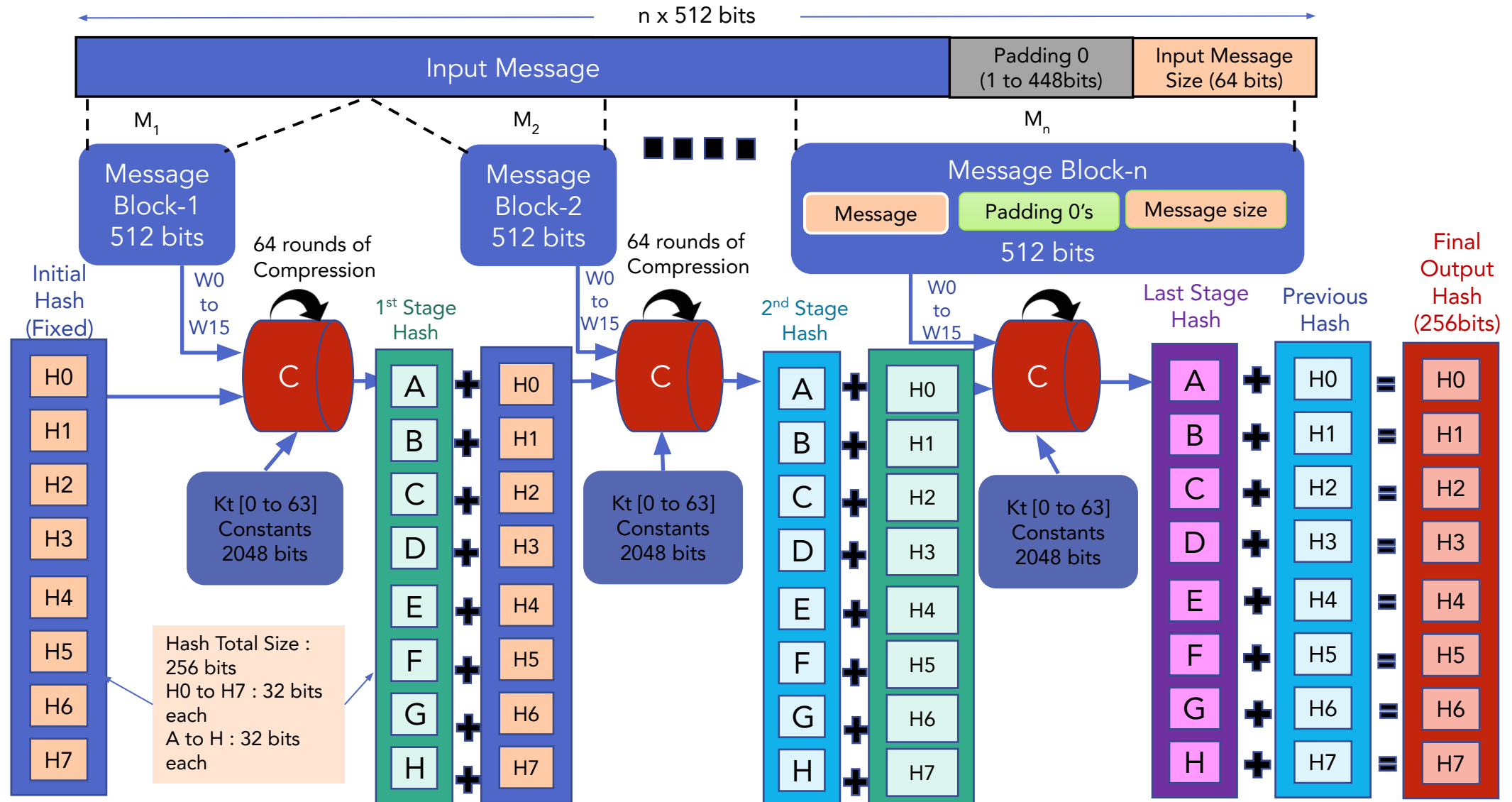


SHA256 Algorithm

❑ Step 1: Append padding bits (1 and 0's)

- A L -bit message M is padded in the following manner:
 - Add a single "1" to the end of M
 - Then pad message with "0's" until the length of message is congruent to 448, modulo 512 (which means pad with 0's until message is 64-bits less than some multiple of 512).

❑ Step 2 : Append message length bits in 0 to 63 bit position

 - Since SHA256 supports until 2^{64} input message size, 64 bits are required to append message length



- L = Length of original message
- P = Padded bits

Append 1
After Message

SHA256 Algorithm

❑ Step 3 : Buffer Initialization

- Initialize message digest (MD) buffers / output hash to these 8 32-bit words

H0 = 6a09e667

H1 = bb67ae85

H2 = 3c6ef372

H3 = a54ff53a

H4 = 510e527f

H5 = 9b05688c

H6 = 1f83d9ab

H7 = 5be0cd19

SHA256 Algorithm

❑ Step 4 : Processing of the message (algorithm)

- Divide message M into 512-bit blocks, $M_0, M_1, \dots M_j, \dots$
- Process each M_j sequentially, one after the other
- Input:
 - W_t : a 32-bit word from the message
 - K_t : a constant array
 - $H_0, H_1, H_2, H_3, H_4, H_5, H_6, H_7$: current MD (Message Digest)
- Output:
 - $H_0, H_1, H_2, H_3, H_4, H_5, H_6, H_7$: new MD (Message Digest)

SHA256 Algorithm

□ Step 4 : Cont'd

- At the beginning of processing each M_j , initialize
(A, B, C, D, E, F, G, H) = (H0, H1, H2, H3, H4, H5, H6, H7)
- Then 64 processing rounds of 512-bit blocks
- Each step t ($0 \leq t \leq 63$): Word expansion for W_t
 - If $t < 16$
 - $W_t = t\text{th}$ 32-bit word of block M_j
 - If $16 \leq t \leq 63$
 - $s_0 = (W_{t-15} \text{ rightrotate } 7) \text{ xor } (W_{t-15} \text{ rightrotate } 18) \text{ xor } (W_{t-15} \text{ rightshift } 3)$
 - $s_1 = (W_{t-2} \text{ rightrotate } 17) \text{ xor } (W_{t-2} \text{ rightrotate } 19) \text{ xor } (W_{t-2} \text{ rightshift } 10)$
 - $W_t = W_{t-16} + s_0 + W_{t-7} + s_1$

SHA256 Algorithm

❑ Step 4: Cont'd

■ K_t constants

$K [0..63] = 0x428a2f98, 0x71374491, 0xb5c0fbcf, 0xe9b5dba5,$
 $0x3956c25b, 0x59f111f1, 0x923f82a4, 0xab1c5ed5, 0xd807aa98,$
 $0x12835b01, 0x243185be, 0x550c7dc3, 0x72be5d74, 0x80deb1fe,$
 $0x9bdc06a7, 0xc19bf174, 0xe49b69c1, 0xefbe4786, 0x0fc19dc6,$
 $0x240ca1cc, 0x2de92c6f, 0x4a7484aa, 0x5cb0a9dc, 0x76f988da,$
 $0x983e5152, 0xa831c66d, 0xb00327c8, 0xbf597fc7, 0xc6e00bf3,$
 $0xd5a79147, 0x06ca6351, 0x14292967, 0x27b70a85, 0x2e1b2138,$
 $0x4d2c6dfc, 0x53380d13, 0x650a7354, 0x766a0abb, 0x81c2c92e,$
 $0x92722c85, 0xa2bfe8a1, 0xa81a664b, 0xc24b8b70, 0xc76c51a3,$
 $0xd192e819, 0xd6990624, 0xf40e3585, 0x106aa070, 0x19a4c116,$
 $0x1e376c08, 0x2748774c, 0x34b0bcb5, 0x391c0cb3, 0x4ed8aa4a,$
 $0x5b9cca4f, 0x682e6ff3, 0x748f82ee, 0x78a5636f, 0x84c87814,$
 $0x8cc70208, 0x90befffa, 0xa4506ceb, 0xbef9a3f7, 0xc67178f2$

SHA256 Algorithm

□ Step 4 : Cont'd

- Each step t ($0 \leq t \leq 63$):

$\Sigma 0$ $S_0 = (A \text{ rightrotate } 2) \text{ xor } (A \text{ rightrotate } 13) \text{ xor } (A \text{ rightrotate } 22)$

Ma $\text{maj} = (A \text{ and } B) \text{ xor } (A \text{ and } C) \text{ xor } (B \text{ and } C)$


$$t_2 = S_0 + \text{maj}$$

$\Sigma 1$ $S_1 = (E \text{ rightrotate } 6) \text{ xor } (E \text{ rightrotate } 11) \text{ xor } (E \text{ rightrotate } 25)$

Ch $\text{ch} = (E \text{ and } F) \text{ xor } ((\text{not } E) \text{ and } G)$

$$t_1 = H + S_1 + \text{ch} + K[t] + W[t]$$
 
$$(A, B, C, D, E, F, G, H) = (t_1 + t_2, A, B, C, D + t_1, E, F, G)$$



SHA256 Algorithm

❑ Step 4 : Cont'd

- Finally, when all 64 steps have been processed, set

$$H0 = H0 + a$$

$$H1 = H1 + b$$

$$H2 = H2 + c$$

$$H3 = H3 + d$$

$$H4 = H4 + e$$

$$H5 = H5 + f$$


$$H6 = H6 + g$$

$$H7 = H7 + h$$

❑ Step 5 : Output


- When all M_j have been processed, the 256-bit hash of M is available in $H0, H1, H2, H3, H4, H5, H6, H7$

SHA-256 Algorithm Overview

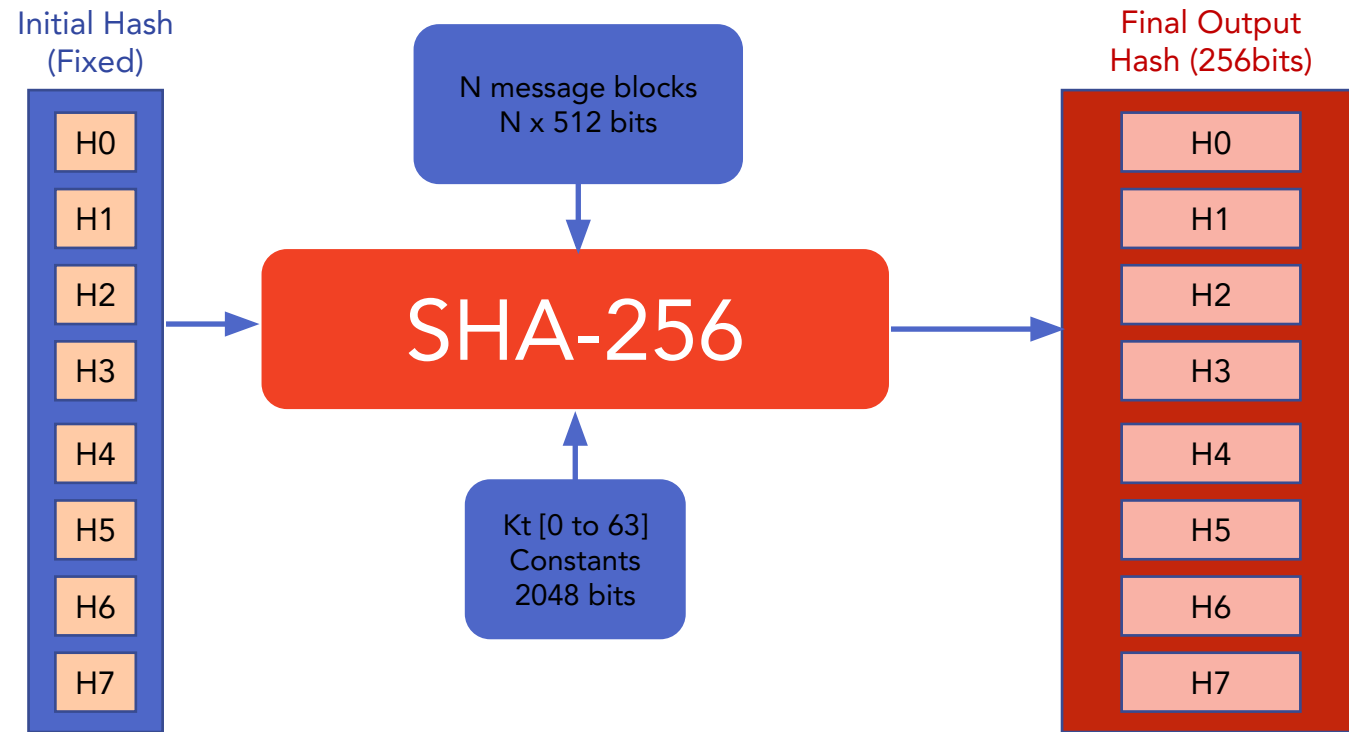


SHA-256: Module Interface

- Wait in idle state for **start**, read message starting at **message_addr** and write final hash {H0, H1, H2, H3, H4, H5, H6, H7} in 8 words to memory starting at **output_addr**
 - message_addr** and **output_addr** are word addresses
- Message size is "hardcoded" to 20 words (640 bits)
- Set **done** to 1 when finished
- Testbench has memory defined named "dpsram[0:16383]" which has all 20 word of input message available

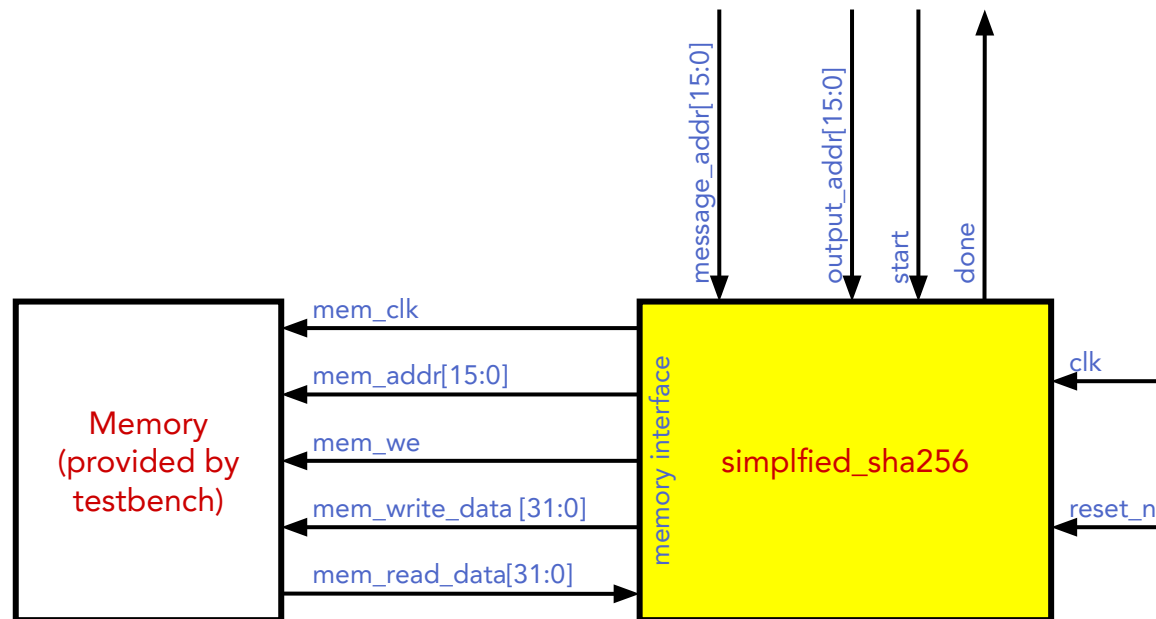

output_addr	H0
output_addr + 1	H1
output_addr + 2	H2
output_addr + 3	H3
output_addr + 4	H4
output_addr + 5	H5
output_addr + 6	H6
output_addr + 7	H7

SHA-256: FSM Design

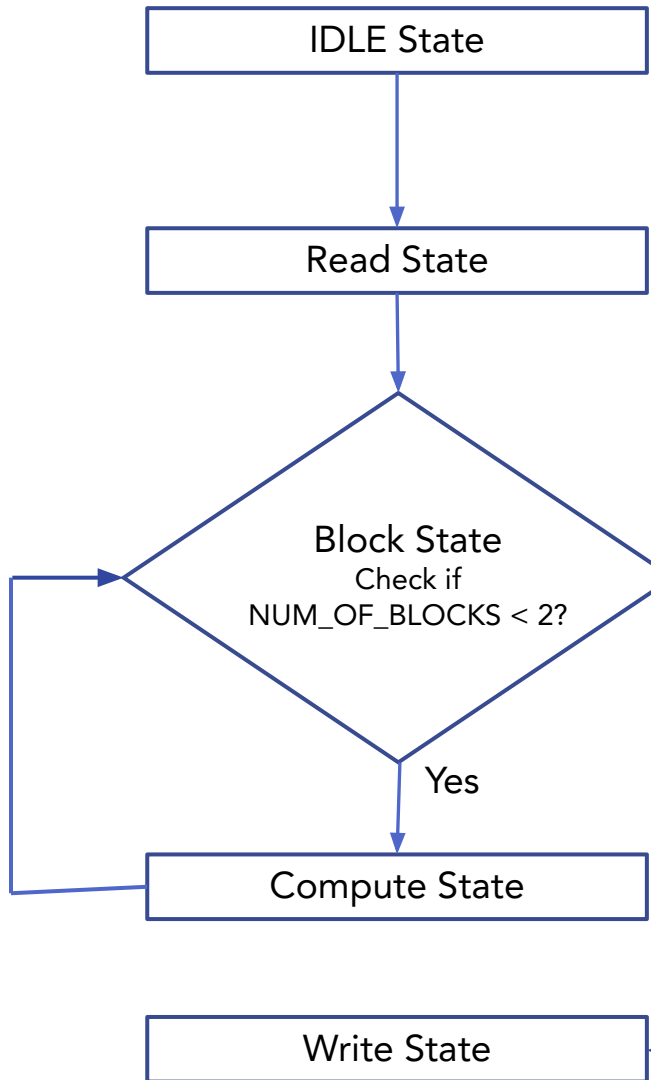

- If start==1, Initialize h0, h1, h2, h3, h4, h5, h6, h7 to initial hash values
- Initialize a, b, c, d, e, f, g, h
- Initialize write enable to memory, memory address offset, curr_addr to first message location in memory, index variables, etc
- Move to read input message FSM state

- Read 640 bits message from testbench memory in chunks of 32bits words (i.e. read 20 locations from memory by incrementing address offset)
- Move to Block creation FSM state

- In Block FSM state, Create two message blocks each of 512 bits
- First message block has first 16 words of input message stored in 'w' array
- Second message block has 4 words of input message, value 1, padding 0 and message size 640
- Assign h0, h1, h2, h3, h4, h5, h6, h7 to a, b, c, d, e, f, g, h respectively
- Check if for both blocks SHA256 operation has been processed and hash is created, if yes then move to WRITE state otherwise move to compute state

- Perform Word expansion of 16 elements of input message block (512 bits) and create total 64 word array each having 32 bits
- Perform 64 rounds of SHA operation to generate hash values in 'a' through 'h' array. Increment number of blocks iteration variable
- Add previous hash values with 'a' through 'h' hash values, go back to BLOCK State

- Write 256 bit hash value stored in h0 to h7 hash variables in testbench memory using output_addr as a starting address location
- Set done = 1 and then move to IDLE state